

## ACHD Final Project- Part 1

### Deliverables (per team):

1. VHDL code of the complete processor and its individual components. (along with testbenches)
2. Screenshots of Functional and Timing Simulation of all the individual components of the processor. (Please use a test bench to simulate)
3. Screenshots of Functional and Timing Simulation of the complete integrated processor. Use the two sample codes provided and show the results (relevant register contents, data memory and program counter value).
4. Demo on FPGA

Submit 2-3 in a single PDF. For VHDL code, only submit your .vhd files.

If SHL or SHR instruction is not part of your specification then remove that line from sample code.

If your specification is byte addressable then modify the stores and loads accordingly.

#### Sample code 1:

000001000000000010000000000000111	--ADDI R1, R0, 7	// R1 = 7
000001000000000010000000000001000	--ADDI R2, R0, 8	// R2 = 8
00000000010000010001100000010000	--ADD R3, R1, R2	// R3 = R1 + R2 =15
111111000000000000000000000000000	--HAL	// HALT

#### Sample code 2:

000001 00000 00001 0000000000000010	--ADDI R1, R0, 2	//R1=R0+2(decimal)
000001 00000 00011 0000000000001010	--ADDI R3, R0, 10	//R3=R0+10(decimal)
000001 00000 00100 0000000000001110	--ADDI R4, R0, 14	//R4=R0+14(decimal)
000001 00000 00101 0000000000000010	--ADDI R5, R0, 2	//R5=R0+2
001000 00011 00100 0000000000000010	--SW R4, 2(R3)	//Mem[R3+2]=R4
001000 00011 00011 0000000000000001	--SW R3, 1(R3)	//Mem[R3+1]=R3
000000 00100 00011 00100 00000 010001	--SUB R4, R4, R3	//R4=R4-R3
000010 00000 00100 0000000000000001	--SUBI R4, R0, 1	//R4=R0-1(decimal)
000000 00011 00010 00100 00000 010010	--AND R4, R2, R3	//R4=R2 and R3
000011 00010 00100 0000000000001010	--ANDI R4, R2, 10	//R4=R2 and 10(decimal)
000000 00011 00010 00100 00000 010011	--OR R4, R2, R3	//R4= R2 or R3
000111 00011 00010 0000000000000001	--LW R2, 1(R3)	//R2=Mem[1+R3]
000100 00010 00100 0000000000001010	--ORI R4, R2, 10	//R4=R2 or 10(decimal)
000000 00011 00010 00100 00000 010100	--NOR R4, R2, R3	//R4= R2 nor R3
000101 00010 00100 0000000000001010	--SHL/ R4, R2, 10	//R4= R2 << 10(decimal)
000110 00010 00100 0000000000001010	--SHR R4, R2, 10	//R4=R2 >> 10(decimal)
001010 00000 00101 1111111111111110	--BEQ R5, R0, -2	
001001 00100 00101 0000000000000000	--BLT R5, R4, 0 --	
001011 00100 00101 0000000000000000	BNE R5, R4, 0 --	
001100 00000000000000000000001010	JMP 20	
111111 00000000000000000000000000	--HAL	